

Jin-Soo Kim  
(jinsoo.kim@snu.ac.kr)

Systems Software &  
Architecture Lab.  
Seoul National University

Fall 2019

# Sequential Processor

Chap. 4.1, 4.3, 4.4



# Introduction


- CPU performance factors
  - Instruction count – Determined by ISA and compiler + algorithm
  - CPI and cycle time – Determined by CPU hardware
- We will examine two RISC-V implementations
  - A simplified (sequential) version
  - A more realistic pipelined version
- Simple subset, shows most aspects
  - Memory reference: ld, sd
  - Arithmetic/logical: add, sub, and, or
  - Control transfer: beq

# Instruction Execution


- PC  $\rightarrow$  instruction memory, fetch instruction
- Register numbers  $\rightarrow$  register file, read registers
- Depending on instruction class
  - Use ALU to calculate:     Arithmetic result  
                                    Memory address for load/store  
                                    Branch comparison
  - Access data memory for load/store
  - PC  $\leftarrow$  target address or PC + 4

**CPU: Datapath + Control**

# CPU Overview

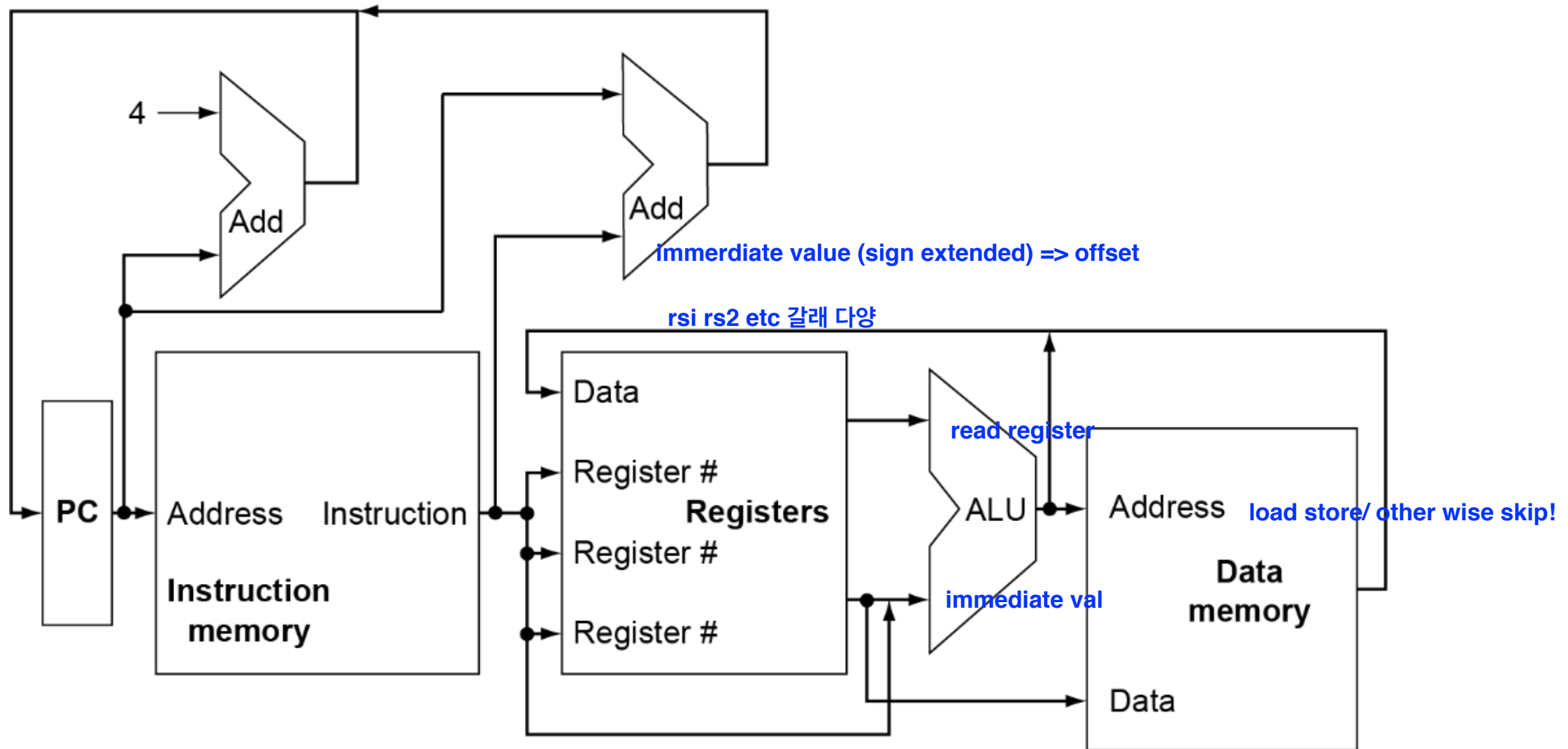


# Multiplexers

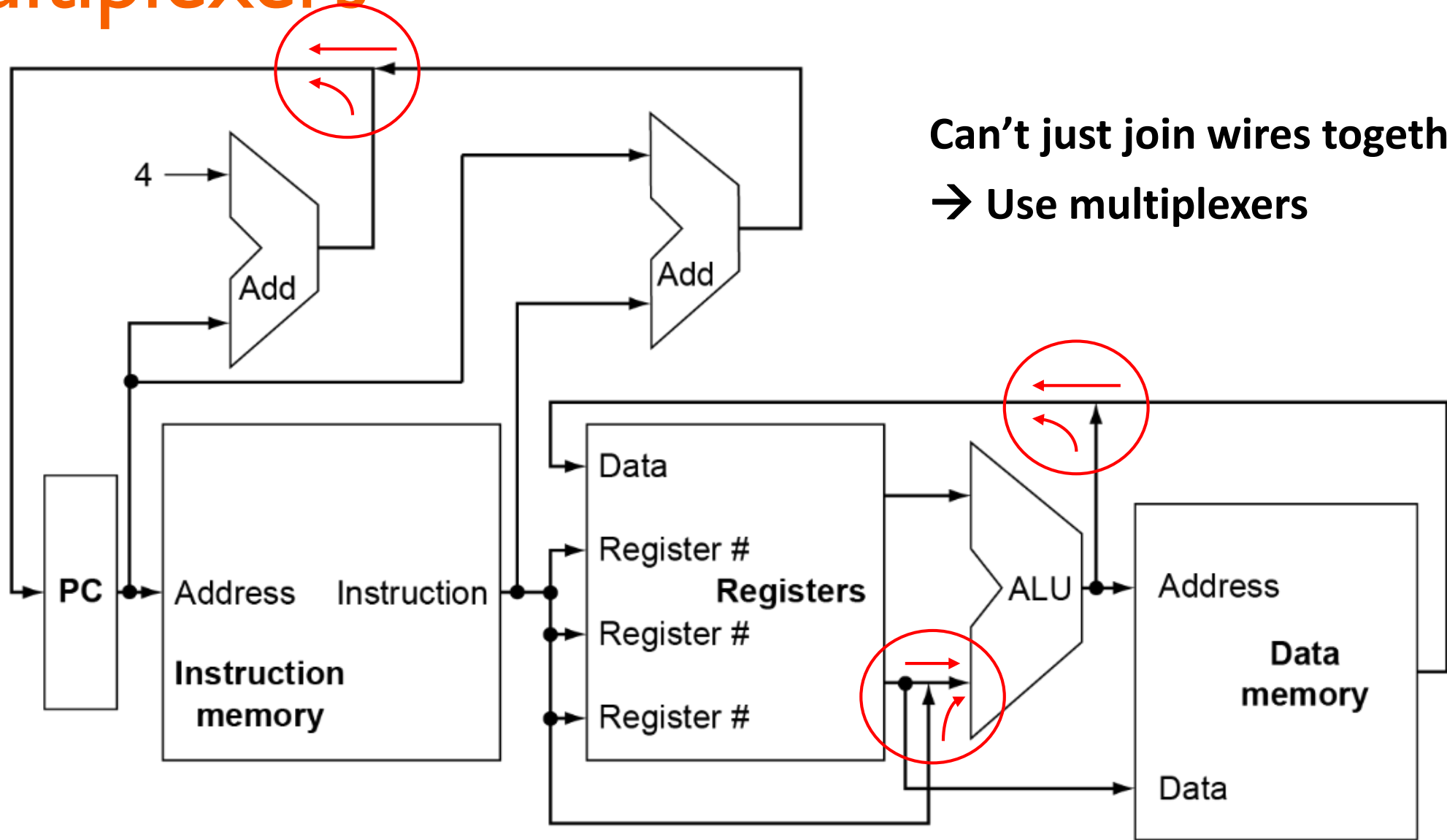

Can't just join wires together  
→ Use multiplexers
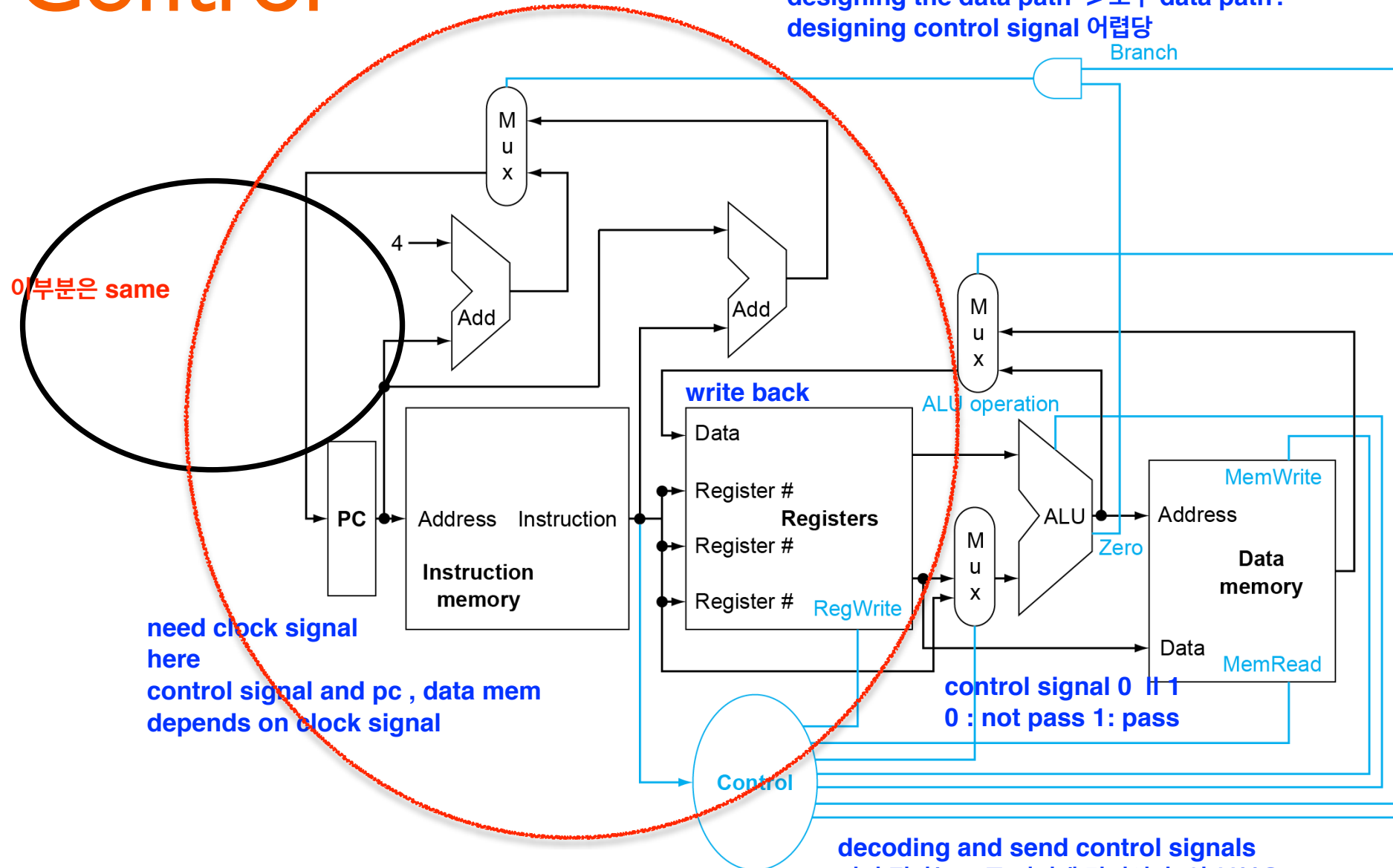
# Control


components : mux adder instruction memory registers data memory ALU etc  
 designing the data path -> 모두 data path?  
 designing control signal 어렵당



# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
  - Registers, ALUs, MUX's, Memories, ...
- We will build a RISC-V datapath incrementally
  - Refining the overview design


# Instruction Fetch

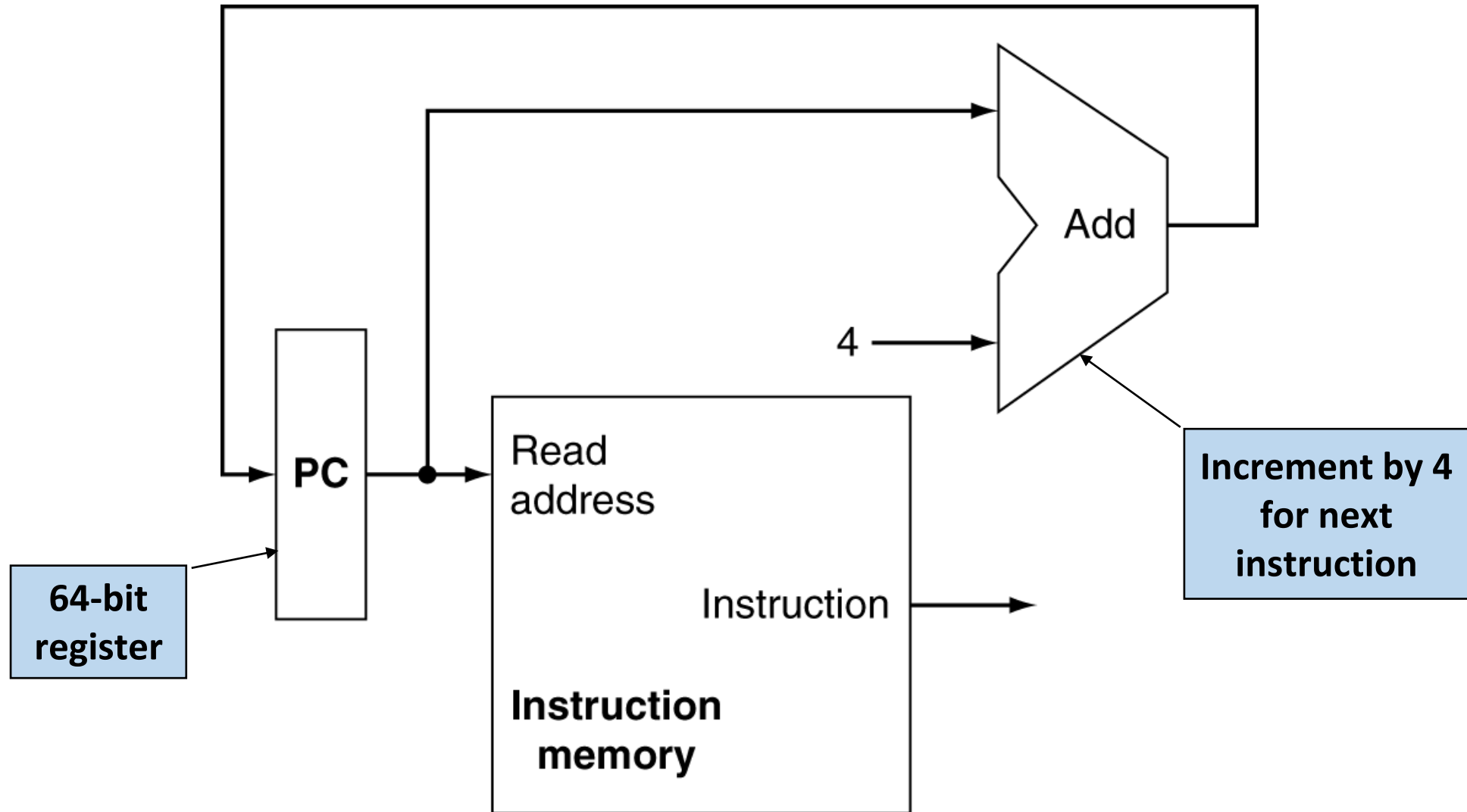



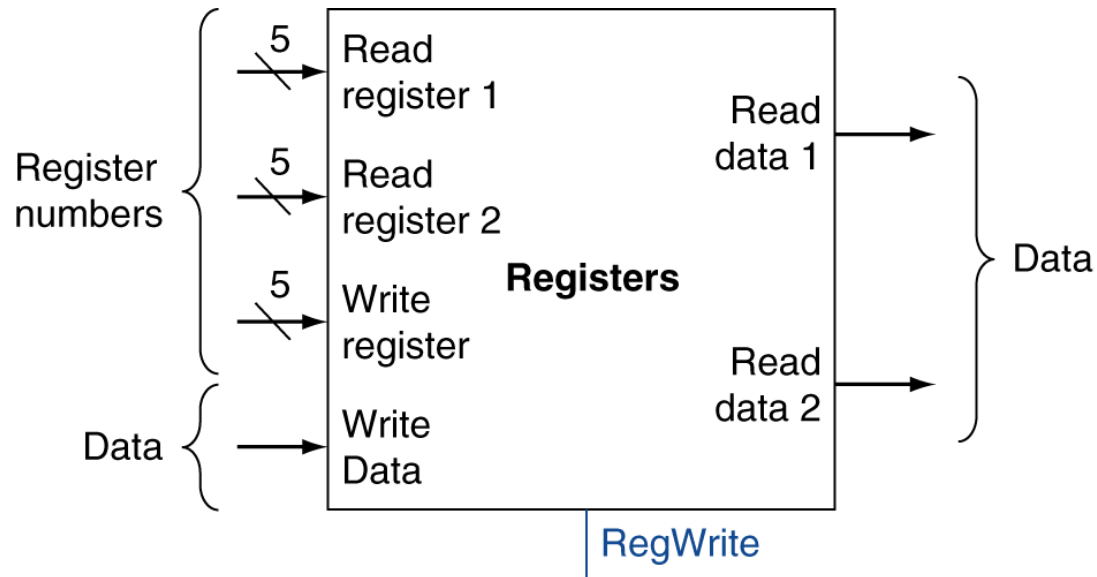
# R-Format Instructions

- Read two register operands
- Perform arithmetic/logical operation
- Write register result




a. Registers

 

b. ALU
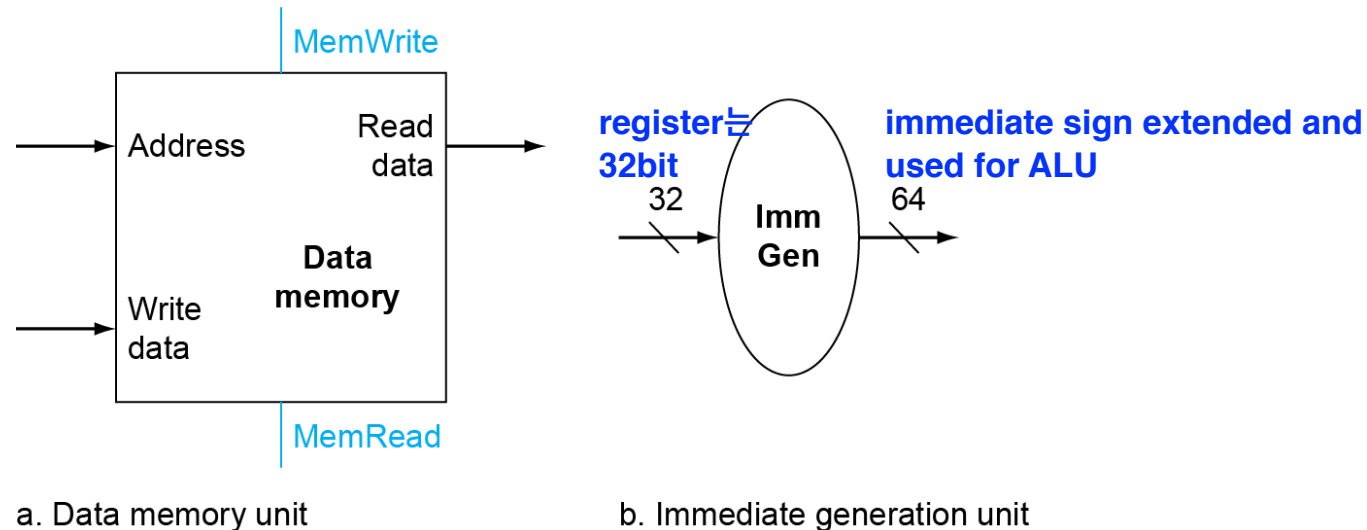
# Load/Store Instructions

- Read register operand
- Calculate address using 12-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




# Branch Instructions

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 1 place (halfword displacement)
  - Add to PC value

branch target  
address


# Branch Instructions (cont'd)

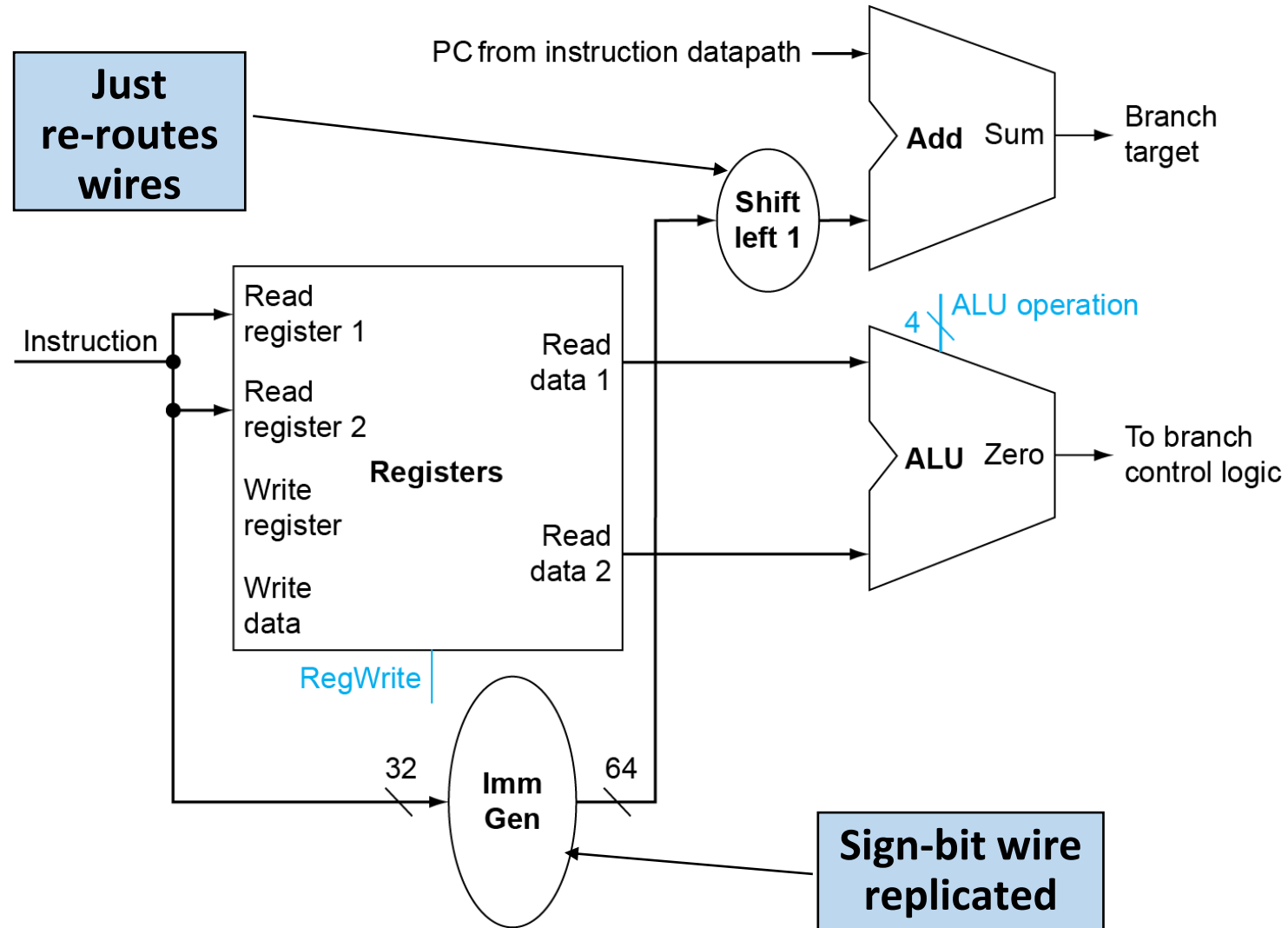


# Composing the Elements

- First-cut datapath does an instruction in one clock cycle
  - Each datapath element can only do one function at a time
  - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

# R-Type/Load/Store Datapath

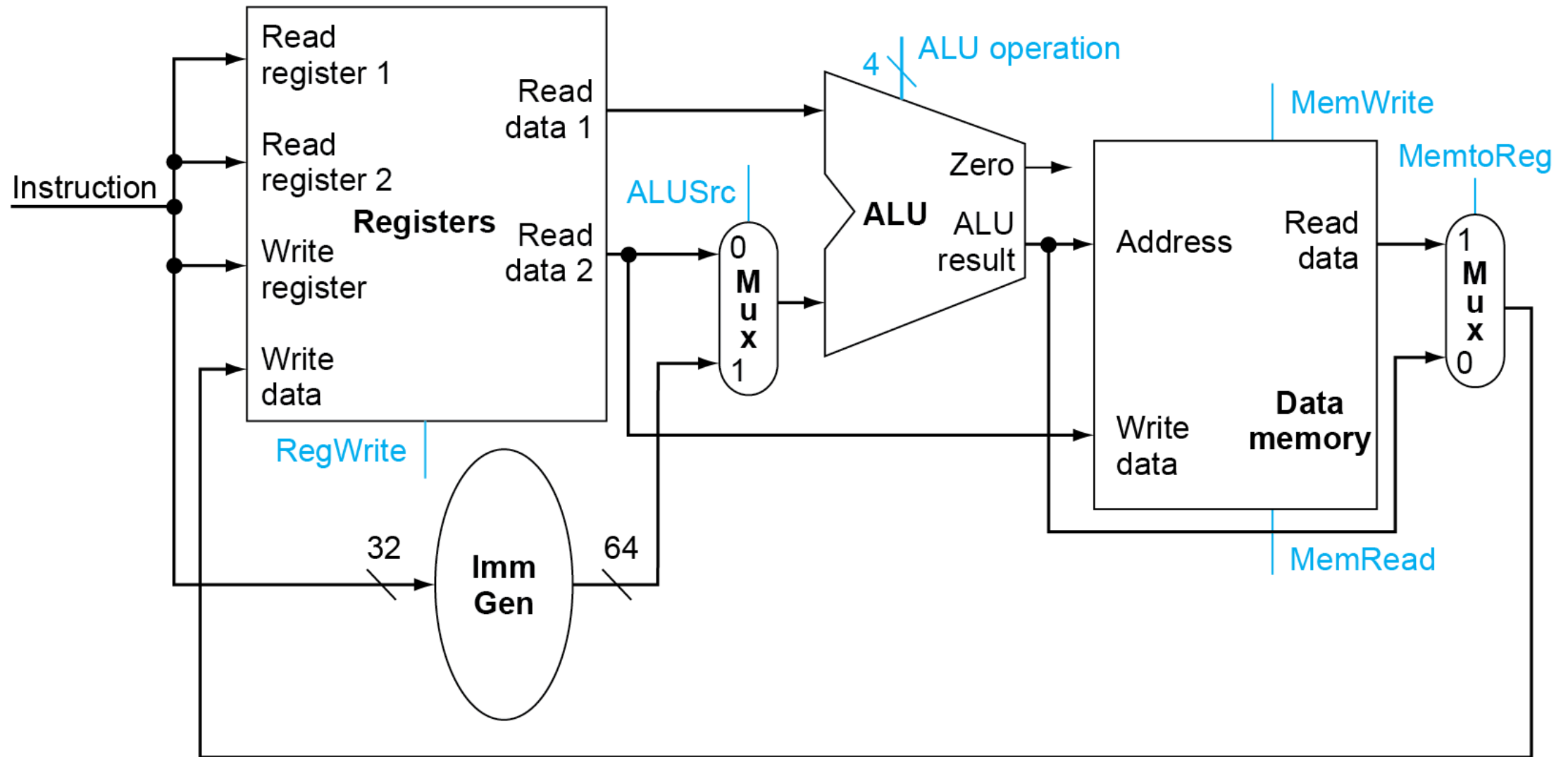

# Full Datapath

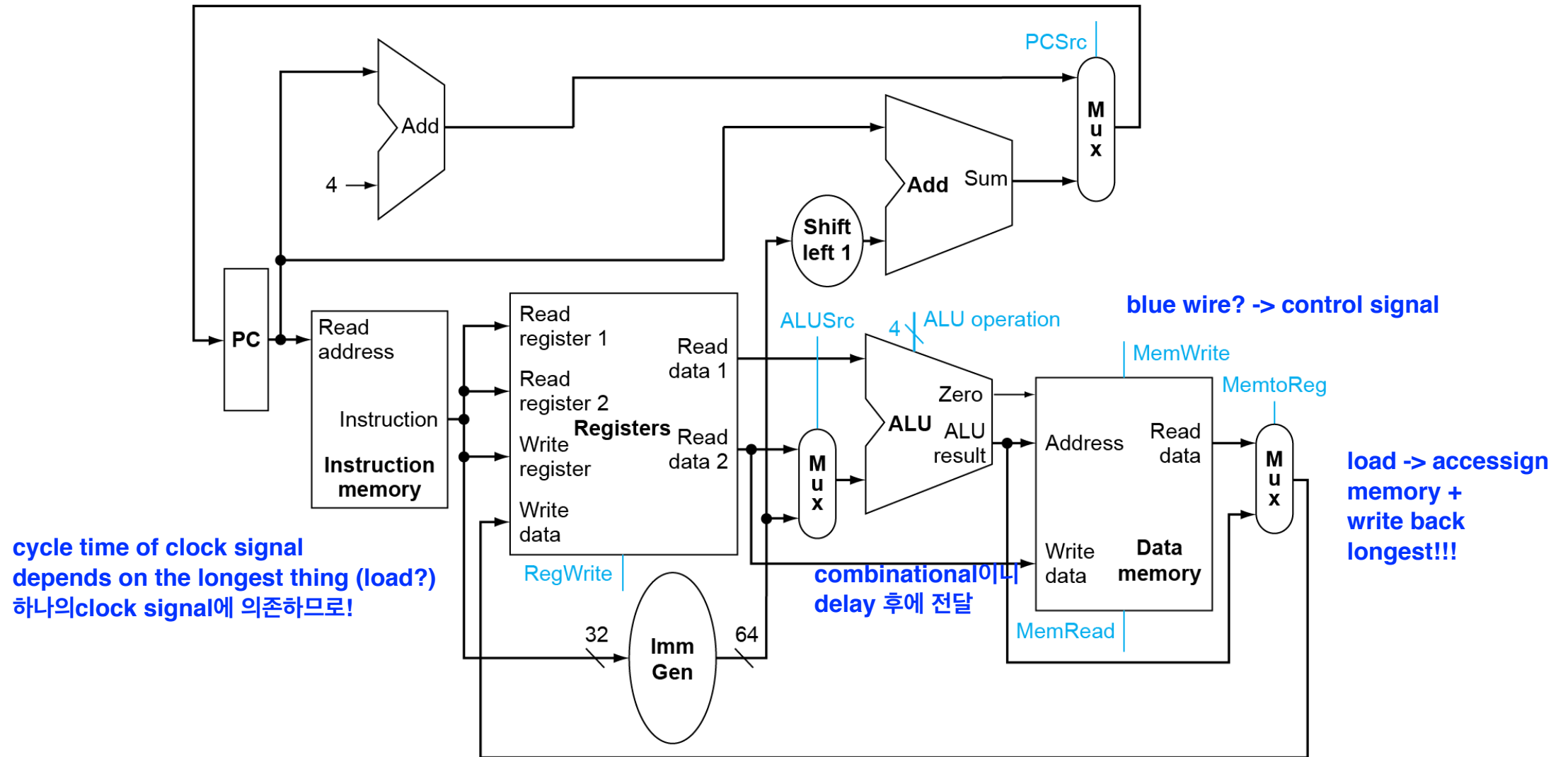

# ALU Control

- ALU used for
  - Load/Store: F = add
  - Branch: F = subtract [check 0 || 1](#)
  - R-type: F depends on opcode

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract



# ALU Control (cont'd)

- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
ld	00	load register	XXXXXXXX	XXX	add	0010
sd	00	store register	XXXXXXXX	XXX	add	0010
beq	01	branch on equal	XXXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001

# The Main Control Unit

- Control signals derived from instruction


immediates 필요하지 않더라도 일단 rs로 해석하고 register 로 보내고 나중에 필요 없으면 버린다.

Name (Bit position)	Fields					
	31:25	24:20	19:15	14:12	11:7	6:0
(a) R-type	funct7	rs2	rs1	funct3	rd	opcode
(b) I-type	immediate[11:0]		rs1	funct3	rd	opcode
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode

left most bit! (always) -> wenn need sign extend replicating sign bit needed!!!

ALUOp		Funct7 field							Funct3 field			Operation
ALUOp1	ALUOp0	I[31]	I[30]	I[29]	I[28]	I[27]	I[26]	I[25]	I[14]	I[13]	I[12]	
0	0	X	X	X	X	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	X	X	X	X	0110
1	X	0	0	0	0	0	0	0	0	0	0	0010
1	X	0	1	0	0	0	0	0	0	0	0	0110
1	X	0	0	0	0	0	0	0	1	1	1	0000
1	X	0	0	0	0	0	0	0	1	1	0	0001


# Datapath with Control

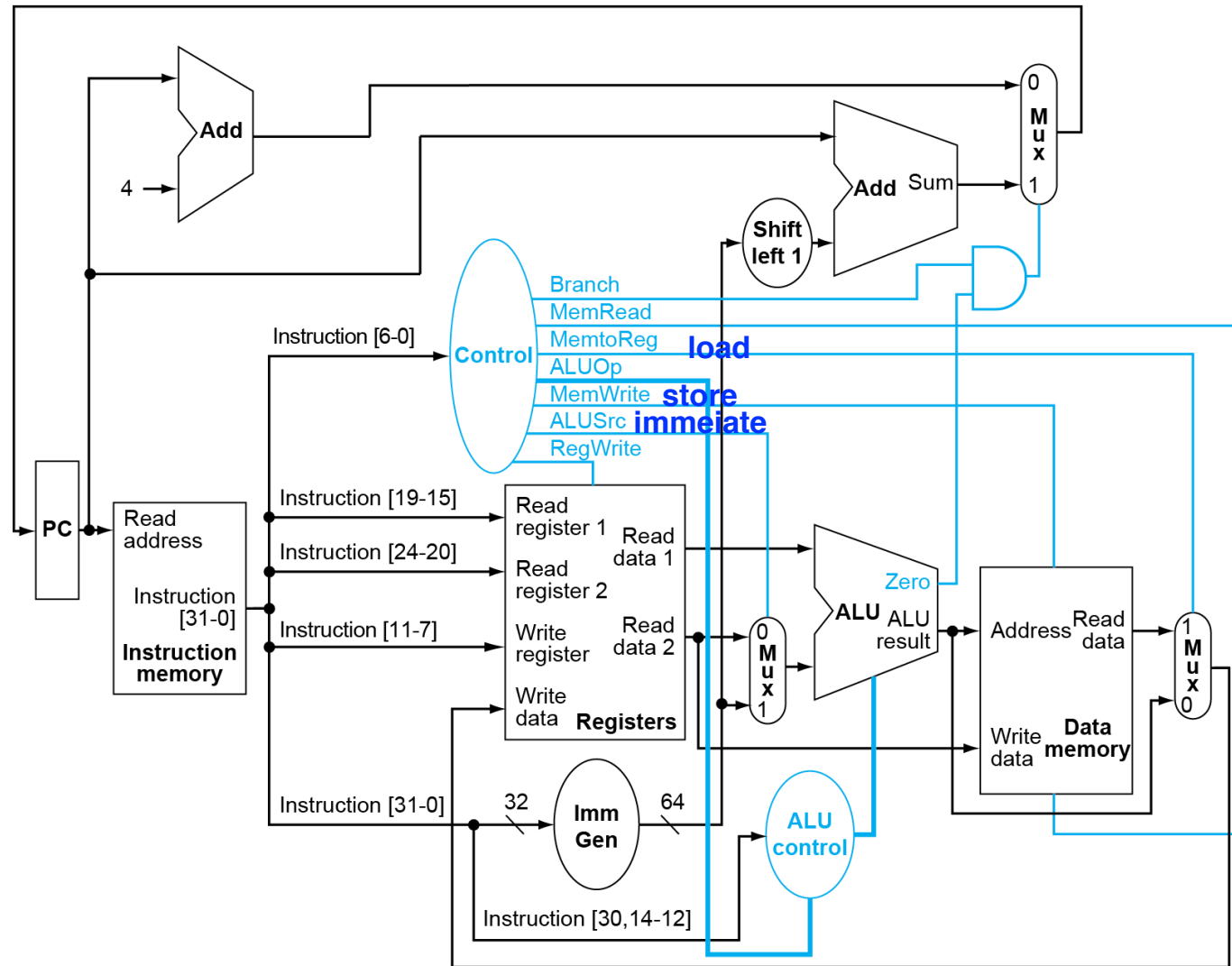


# R-Type Instruction
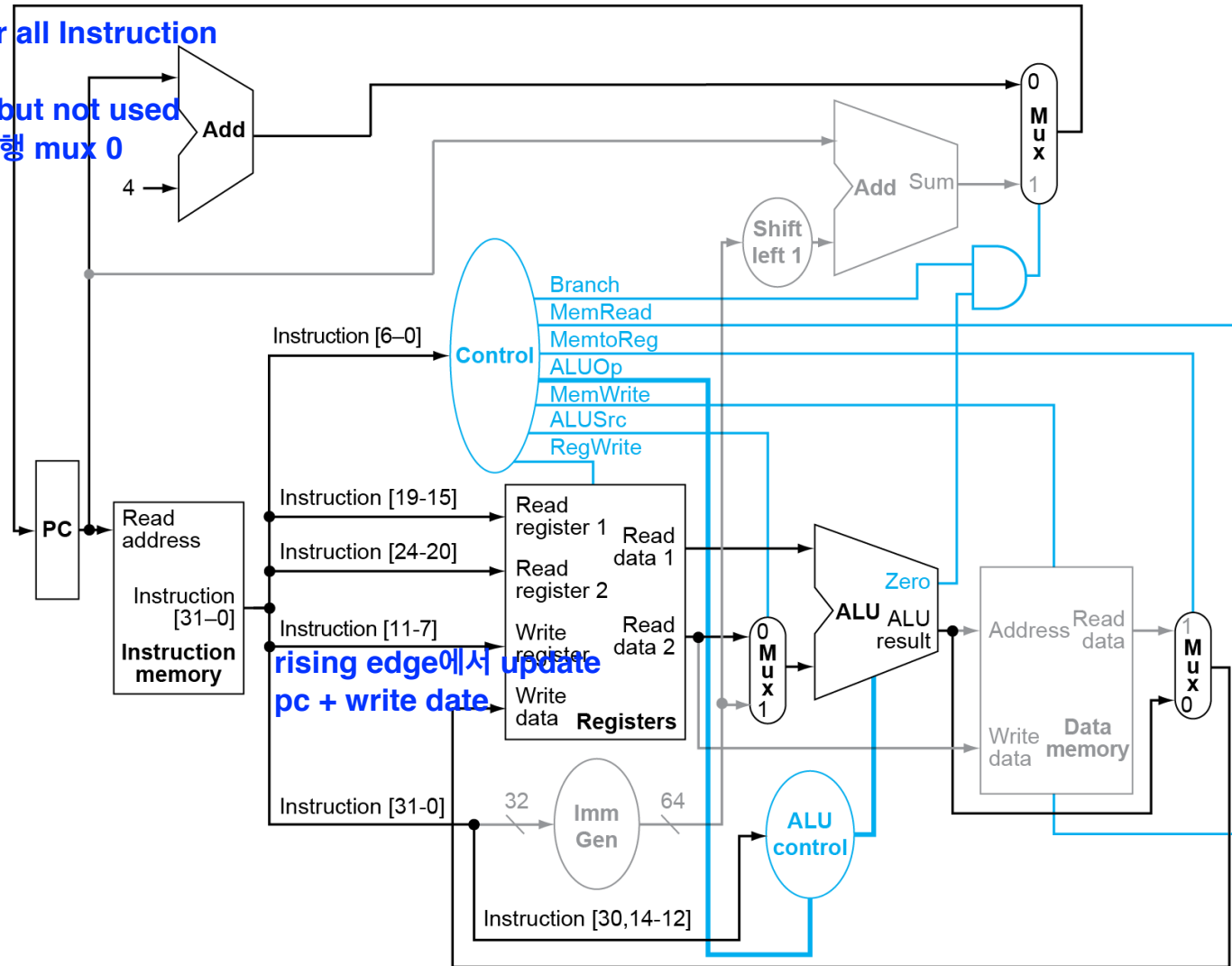
## ALU


accessing은 same for all Instruction  
decoding peparing  
immediate prepared but not used  
rs1 rs2 passed alu 실행 mux 0



# Load Instruction

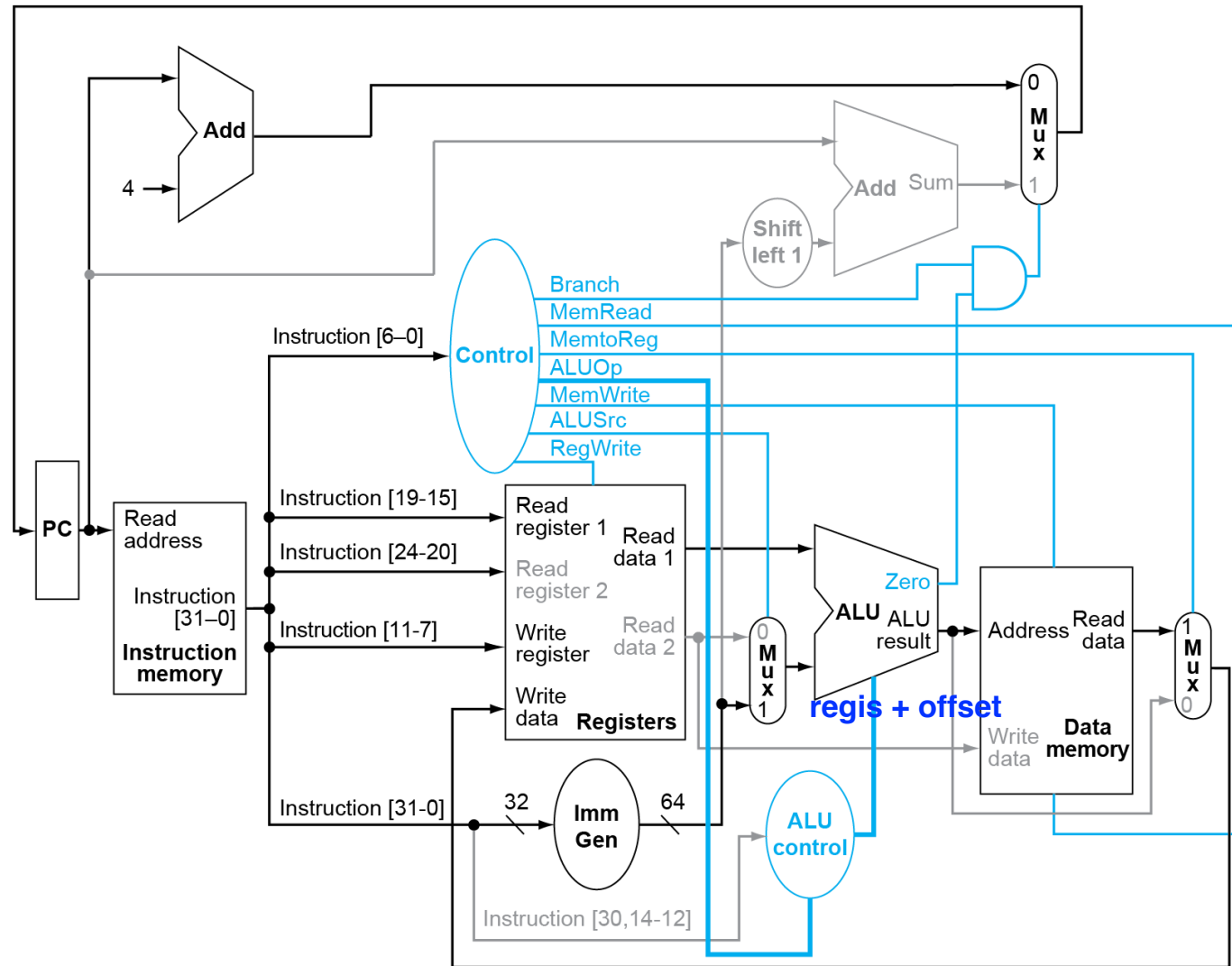

# BEQ Instruction

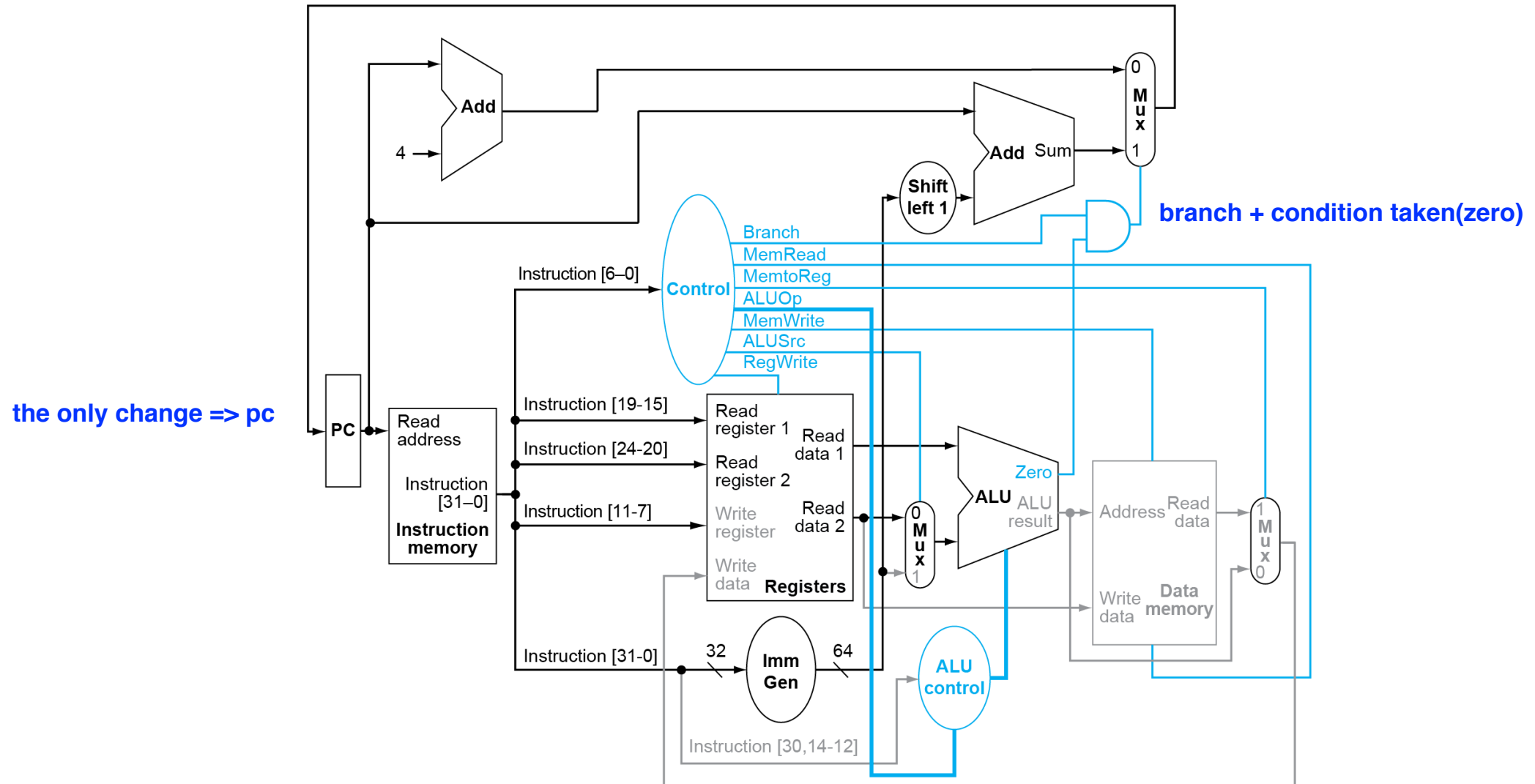

# Performance Issues

- Longest delay determines clock period
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle: Making the common case fast
- We will improve performance by pipelining