

Lab. o8

Logic Design Lab.

Fall 2019

Prof. Sungjoo Yoo

(yeonbin@snu.ac.kr)

TA. Hyunsu Kim

(gustnxodjs@gmail.com)

TA. Hyunyoung Jung


(gusdud1500@gmail.com)

Overview

- FSM: Moore & Mealy Machine
- Verilog FSM Implementation Example
- Lab
- Homework


FSM: Moore & Mealy Machine

- Definition of Moore & Mealy Machine

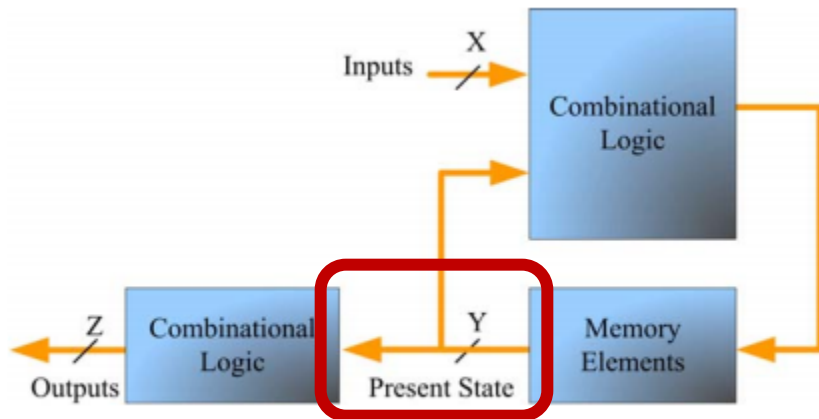

Moore machine

 - Outputs are computed via a function of current state only
- Output delayed by one clock period



Mealy machine

- Outputs are computed via a function of current state and input values

FSM: Moore & Mealy Machine


■ State Transition Diagram

0, 1: input

a, b: output


s0, s1: state

output depends
only on prior state

 

Moore machine

 output depends
both on prior state AND input




Mealy Machine

Verilog FSM Implementation Example

- Manchester Encoding

0: 

1: 


 


Serial Data Code Conversion


NRZ-Code to Manchester-Code

Mealy machine implementation

  - Use Clock2, twice the frequency of the basic clock
 - If the NRZ bit is 0 (1), it will be 0 (1) for two Clock2 periods



Present State	Next State		Output Z	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₂	0	1
S ₁	S ₀	-	1	-
S ₂	-	S ₀	-	0

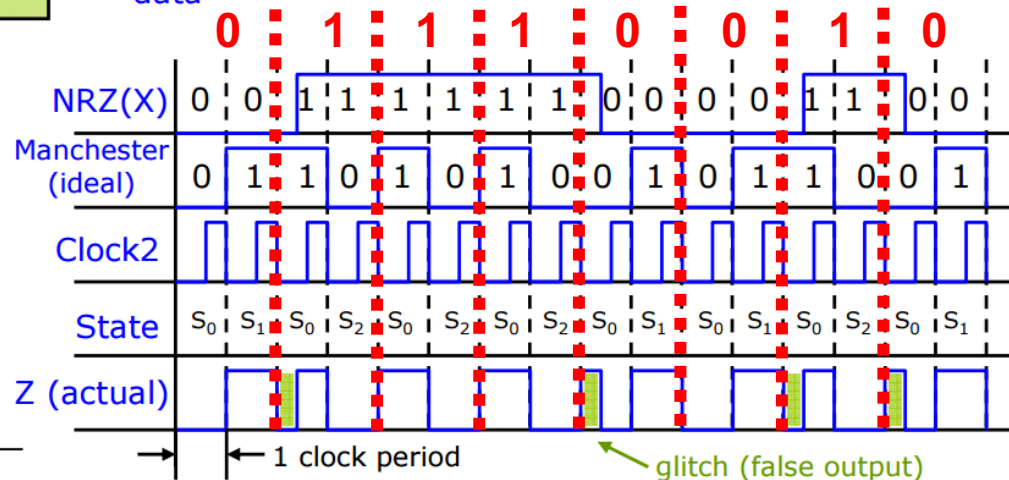


Serial Data Code Conversion


NRZ-Code to Manchester-Code

Moore machine implementation

 glitch있어도 상관없다. ->
state 절대적/ input-output
mealy 는 glitch 영향




Present State	Next State		Present Output Z
	X=0	X=1	
S ₀	S ₁	S ₃	0
S ₁	S ₂	-	0
S ₂	S ₁	S ₃	1
S ₃	-	S ₀	1

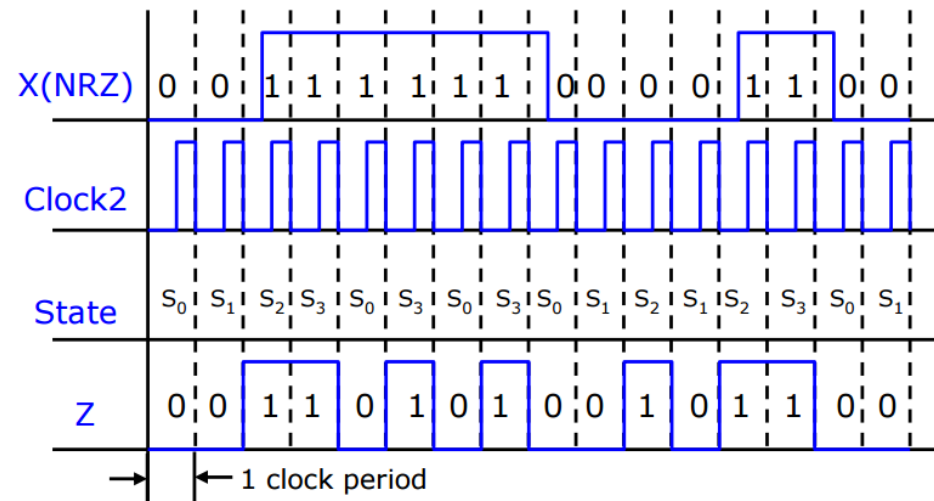

Output delayed by one clock period

Verilog FSM Implementation Example

- Mealy machine

 


```
module Manchester_Mealy(
    input reset,
    input in,
    input clk2,
    output out,
    output reg [1:0] state
);
    reg [1:0] next;
    localparam s0=0, s1=1, s2=2;

    always@(posedge clk2)
        state <= reset ? s0 : next;

    always@(state or in)
        case(state)
            s0:
                next <= ~in ? s1 :
                    in ? s2 : 2'bx;
            s1:
                next <= s0;
            s2:
                next <= s0;
            default:
                next <= 2'bx;
        endcase

    assign out = (state==s0)&&(in) || (state==s1)&&(~in);


endmodule
```

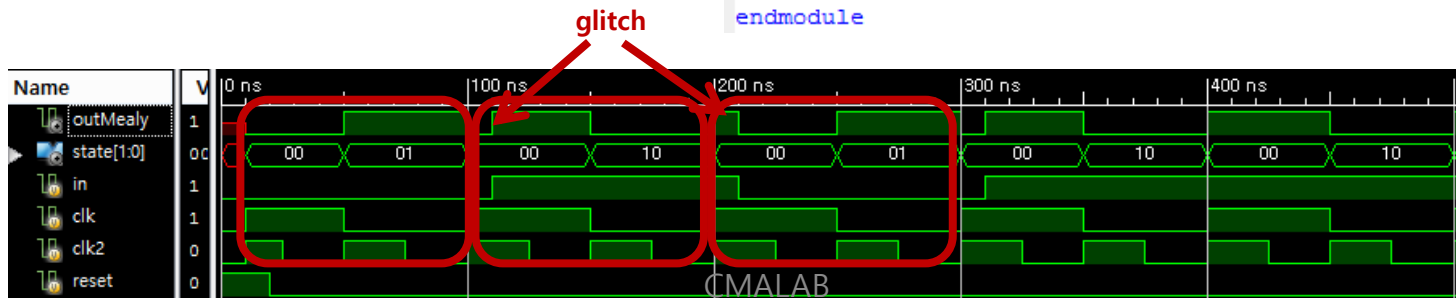

- Output change is NOT synchronous with state change; output can change during one state

Verilog FSM Implementation Example


- Moore machine

 

```
module Manchester_Moore(
    input reset,
    input in,
    input clk2,
    output out,
    output reg [1:0] state
);
    reg [1:0] next;
    localparam s0=0,s1=1,s2=2,s3=3;

    always@(posedge clk2)
        state <= reset ? s0 : next;


    always@(state or in)
        case(state)
            s0, s2:
                next <= ~in ? s1 : s3;
            s1:
                next <= s2;
            s3:
                next <= s0;
            default:
                next <= 2'bx;
        endcase
    assign out = (state==s2) || (state==s3);
endmodule
```

 

- Output change is synchronous with state change; output doesn't change during one state
- Same as synchronous Mealy


Today

 - Implement the vending machine described in Lecture07_FSM slide p19-p31 in Verilog and load it on the Logic Design Board
 - Implement it as a **Mealy** machine and **Moore** machine
 - Discuss the difference of two types of implementation
 - Difference between Mealy and Moore style



Homework

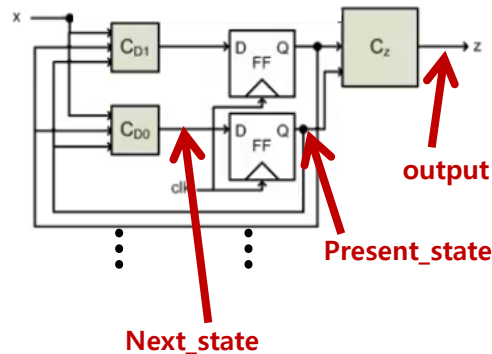1. Implement and simulate '010' string recognizer in **Schematic** using Xilinx ISE
 - **1 bit input, 1 bit output**
 - For all other string that isn't '010', the output must be '0'
 - Use D F/Fs to represent states
 - Test with input '**0100101001101011**' to verify your circuit
- (TIP) Follow the steps below
 1. Draw a state transition diagram and a state transition table
 2. Specify D F/F inputs and one 1-bit output
 3. Draw a circuit block diagram with combinational logic blocks and D F/F like below:



Homework

2-1. Implement your string recognizer **in Verilog**

2-2. **Try to** test your string recognizer on the Logic Design Board

- If possible, test with input '**0100101001101011**' to verify your implementation
- If not, discuss the problems and possible solutions
 - Ex) What is the problem, how to fix the problem, etc.
- You may get full score if you can discuss (or fix) the problem **properly**, although your design does not work on the FPGA Board!

3. Write a report

- # of pages doesn't matter
- All the files related experiments should be submitted
- The file size should **be less than 50MB**
- **Due : 11 Nov. (Before class begins at 7:00pm)**